
 


CSC 565 – Computer System Architecture
Deliverable 2
 Cason Konzer

 ◦ **BLOCK DIAGRAM WITH INPUT OUTPUT PINS**



◦ **CLOCK SIGNAL**

External Clock used for flexibility, and so the programmer knows when to read values on the output bus. (Realistic implementation supports both internal and external clock).

- **NUMBER OF REGISTERS**

Register	Description
IR	Instruction Register (Also Holds Flags)
R0	Register 0
R1	Register 1

3 Registers (Data Out is coded as a register)

- **FLAGS**

Supporting Signed and Overflow, Overflow only relevant for SUB instructions, Signed supported for both SUB and OR

- **OTHER CONTROL REGISTERS THAT WILL BE NEEDED TO PERFORM OPERATIONS**

Use extra bits in IR to hold flags from ALU output, as well as pass 'instruction' flags specifying operands, operation, and output destinations.

- **A DRAFT OF THE INSTRUCTION SET**

Instruction/Flag Bit Encoding

OVF	SGN	OR	SUB	OPO 1	OPO 0	DST 1	DST 0
Overflown Output	Signed Output	ALU flag to use OR	ALU flag to use SUB	Operand 1	Operand 0	Destination 1	Destination 0
<i>BIT 7</i>	<i>BIT 6</i>	<i>BIT 5</i>	<i>BIT 4</i>	<i>BIT 3</i>	<i>BIT 2</i>	<i>BIT 1</i>	<i>BIT 0</i>

Destination Encoding

DST 1	DST 0	ALU Write Back Register(s)
0	0	No Write Back (only bus)
0	1	Write Back to R0
1	0	Write Back to R1
1	1	Write Back to R0 & R1

ALU Encoding

OR	SUB	ALU Operation
0	0	unused
0	1	Integer Subtraction
1	0	Logical Or
1	1	unused

Operation Encoding

OPO 1	OPO 0	Output (* is the operation)
0	0	$R0 * R0$
0	1	$R1 * R0$
1	0	$R0 * R1$
1	1	$R1 * R1$

Output Flag Encoding

OVF	SGN	Characteristics
0	0	Operation has not overflow and output has positive sign
0	1	Operation has not overflow and output has negative sign
1	0	Operation has overflow and output has positive sign
1	1	Operation has overflow and output has negative sign

Enable Encoding

ENA 1 (BIT 1)	ENA 0 (BIT 0)	Enabled Registers
0	0	None (required for ALU output loads)
0	1	R0
1	0	R1
1	1	IR

◦ TIMING DIAGRAM FOR THE FOLLOWING INSTRUCTIONS

// RESET ALL REGISTERS

// LOAD FF INTO R0

// LOAD 00 INTO R1

// DATA_OUT, $R0, R1 = R0 \mid R1 = FF$

// NO OP

// DATA_OUT, $R0, R1 = R0 - R1 = 00$

// NO OP

// NO OP

